

# Chapter 22

## Basic Electrical Tests



Name \_\_\_\_\_

Date \_\_\_\_\_

Instructor \_\_\_\_\_

Score \_\_\_\_\_

**Objective:** After studying this chapter, you will be able to use a systematic approach to find and correct electrical problems and explain causes of basic circuit problems given their symptoms.

---

### Electrical Diagnosis and Repair

1. \_\_\_\_\_ involves using a logical sequence of steps to find the source of an electrical problem. \_\_\_\_\_

2. Due to the complexity of the electronic devices and electrical circuits in late-model vehicles, a(n) \_\_\_\_\_ approach to troubleshooting should never be used. \_\_\_\_\_

3. Describe the systematic approach to troubleshooting.

---

---

---

---

---

4. What questions should you ask when verifying symptoms of a vehicle?

---

---

---

---

---

5. If the right headlight is not working but the left one is working, what should you check?

---

---

6. If only one component does not work, where should you start your tests?

---

---

7. If more than one component does not work, where should you start your tests?

\_\_\_\_\_

\_\_\_\_\_

## Types of Circuit Problems

8. What are the four basic types of circuit problems?

\_\_\_\_\_


\_\_\_\_\_

\_\_\_\_\_

For questions 9–12, match the following terms and identifying phrases.

- |   |                             |
|---|-----------------------------|
| _____ 9. A conductor accidentally touching ground or another conductor. | (A) Open circuit            |
| _____ 10. Occurs only under certain conditions.                         | (B) High circuit resistance |
| _____ 11. A complete break or disconnection in the circuit.             | (C) Intermittent problem    |
| _____ 12. Reduces, but does not stop, current.                          | (D) Short circuit           |

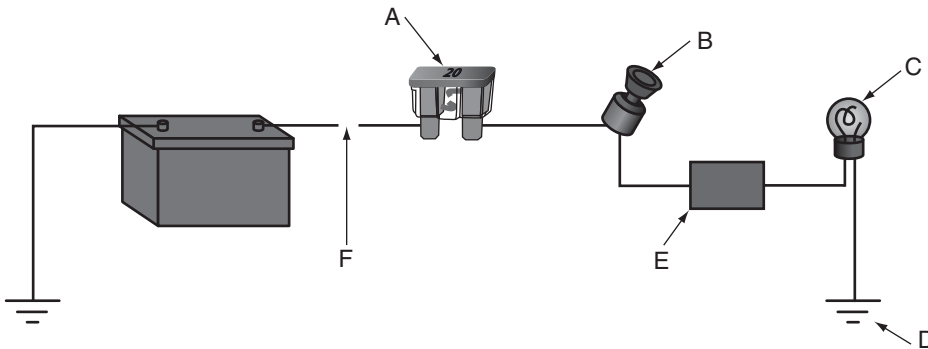13. Identify the sources of opens and breaks in the circuit shown.



- |           |           |
|-----------|-----------|
| (A) _____ | (D) _____ |
| (B) _____ | (E) _____ |
| (C) _____ | (F) _____ |

## Using Test Devices

14. A(n) \_\_\_\_\_ is a piece of wire with alligator clips used to bypass components or to apply voltage to a component or section of a circuit. \_\_\_\_\_
15. (Never, Always) \_\_\_\_\_ use a jumper wire to bypass a high-resistance component, a fuse, or a circuit breaker. \_\_\_\_\_
16. Most test lights have a sharp \_\_\_\_\_ for touching conductors and an alligator clip for grounding. \_\_\_\_\_

Name \_\_\_\_\_

- 17. A self-powered test light, or continuity tester, has an internal \_\_\_\_\_. \_\_\_\_\_
- 18. An inductive wire tracer uses a(n) \_\_\_\_\_ and an inductive pickup to find shorts. \_\_\_\_\_

## Using a Multimeter

- 19. Define *multimeter*.  
 \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_
- 20. Describe what a multimeter does.  
 \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

For questions 21–23, match the following terms and identifying phrases.

- |       |                                     |               |
|-------|-------------------------------------|---------------|
| _____ | 21. Measures current.               | (A) Voltmeter |
| _____ | 22. Measures electrical pressure.   | (B) Ohmmeter  |
| _____ | 23. Measures resistance to current. | (C) Ammeter   |
- 
- 24. Most digital meters are \_\_\_\_\_, meaning that they automatically change to the correct scale. \_\_\_\_\_
  - 25. To avoid blowing a fuse in the ammeter, make sure the possible amp reading is \_\_\_\_\_ the rating of the ammeter. \_\_\_\_\_
  - 26. The bar graph on a digital-analog multimeter serves as a(n) \_\_\_\_\_ display that can show rapid changes in readings. \_\_\_\_\_
  - 27. A fully charged 12-volt battery should have \_\_\_\_\_ volts. \_\_\_\_\_
  - 28. A voltage drop measurement determines the \_\_\_\_\_ of a wire or component. \_\_\_\_\_
  - 29. What is the benefit of using a voltage drop measurement?  
 \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

30. What does infinite resistance mean?

---

---

---

31. A perfect electrical path that exists between the test points means \_\_\_\_ resistance.

---

32. A problem producing a drag on the motor, such as bad armature bearings or a short in a winding, suggests (low, high) \_\_\_\_ current draw.

---

33. Burned motor brushes, poor terminal connections, or a bad ground suggests (low, high) \_\_\_\_ current draw.

---

34. Name three rules to follow when using multimeters.

---

---

---

---

---

---

---

---

---

---

---

## Basic Component Tests

35. A (good, bad) \_\_\_\_ connector has little or no resistance across its terminals.

---

36. A(n) \_\_\_\_ can be used to check for power on both sides of a connector.

---

37. A good variable resistor should exhibit a (fast, slow, gradual) \_\_\_\_ change in resistance as you turn its shaft or move its slide.

---

\_\_\_\_ 38. A switch can be tested by using a(n):

- (A) test light
- (B) voltmeter
- (C) ohmmeter
- (D) All of the above.

39. Give two examples of a transducer switch.

---

---

---

Name \_\_\_\_\_

- \_\_\_\_\_ 40. A(n) \_\_\_\_\_ is normally used to check a temperature switch because the leads to the switch can be disconnected easily.
- (A) test light
  - (B) voltmeter
  - (C) ohmmeter
  - (D) Any of the above.
41. A quick way of checking a temperature switch and its \_\_\_\_\_ circuit is to \_\_\_\_\_ it.
- \_\_\_\_\_ 42. A fuse can be checked using a(n) \_\_\_\_\_.
- (A) test light
  - (B) voltmeter
  - (C) ohmmeter
  - (D) Both A & B.
43. If a fuse is blown, you should check for a(n) \_\_\_\_\_.
44. Why are capacitors used?
- \_\_\_\_\_
- \_\_\_\_\_
- \_\_\_\_\_
- \_\_\_\_\_
- \_\_\_\_\_ 45. A capacitor can be tested using a(n) \_\_\_\_\_.
- (A) test light
  - (B) voltmeter
  - (C) ohmmeter
  - (D) Both A & B.
46. When using an ohmmeter for testing, a diode should \_\_\_\_\_ have \_\_\_\_\_ resistance in one direction and \_\_\_\_\_ resistance in the other.
47. \_\_\_\_\_ can be used to clean oil and grease from \_\_\_\_\_ components before soldering.
48. \_\_\_\_\_ can be used to find intermittent problems in \_\_\_\_\_ electronic components.