

Automotive Technology


Wiring Diagram Practice

Maze VII

Name _____ Date _____ Period _____



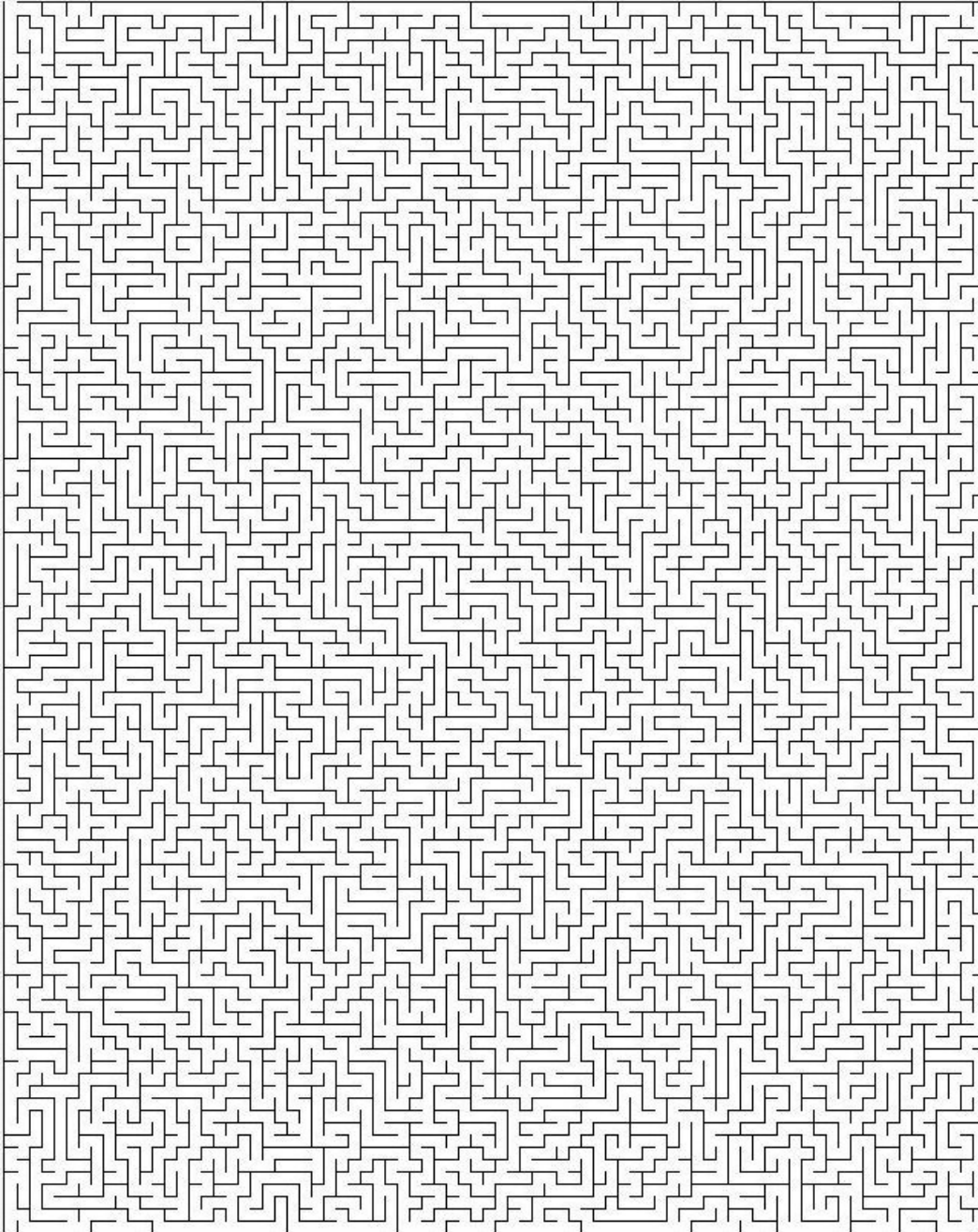Solve the maze using a highlighter marker making no mistakes!



Maze VII / 09-18-11 / vdb

