

**Automotive Technology**  
**Simple Circuits Worksheet II**

-Series and Parallel Circuits-

Name _____ Date _____ Period/Team _____	
<b>Copy the schematics from the whiteboard for each circuit below, have instructor check your drawing, then build each circuit (<i>have instructor check your circuit before turning on power</i>)</b>	
<b>1. Parts used:</b> _____ _____	<b>2. Parts used:</b> _____ _____
<b>Instructor Signature:</b>	<b>Instructor Signature:</b>
<b>3. Parts used:</b> _____ _____	<b>4. Parts used:</b> _____ _____
<b>Instructor Signature:</b>	<b>Instructor Signature:</b>