

Automotive Technology

Simple Circuits Worksheet 5B

-Even More Complex Circuits-
Simple Brake and Turn Signals

Name _____ Date _____ Period/Team _____

Copy the schematic from the power point for this circuit below, have instructor check your drawing, then build the circuit (*do not turn on power until instructor checks your circuit*)

Instructor Signature: