

Automotive Technology
Simple Circuits Worksheet III

-Relay Circuits-

Name _____ Date _____ Period/Team _____

Copy the schematics from the whiteboard for each circuit below, have instructor check your drawing, then build each circuit (*have instructor check your circuit before turning on power*)

1. Parts used: _____

2. Parts used: _____

Instructor Signature:

Instructor Signature:

3. Parts used: _____

4. Parts used: _____

Instructor Signature:

Instructor Signature: