

**Automotive Technology**  
**Simple Circuits Worksheet V**

-Even More Complex Circuits-

Name \_\_\_\_\_ Date \_\_\_\_\_ Period/Team \_\_\_\_\_

Copy the schematics from the power point for each circuit below, have instructor check your drawing, then build each circuit (*do not turn on power until instructor checks your circuit*)

**1. Parts used:** \_\_\_\_\_  
\_\_\_\_\_

**2. Parts used:** \_\_\_\_\_  
\_\_\_\_\_

**Instructor Signature:**

**Instructor Signature:**

**3. Parts used:** \_\_\_\_\_  
\_\_\_\_\_

**4. Parts used:** \_\_\_\_\_  
\_\_\_\_\_

**Instructor Signature:**

**Instructor Signature:**